

Question Paper Code : 323253

B.E./B.Tech. DEGREE EXAMINATIONS April/May 2024

Second Semester

Electronics and Communication Engineering

GE23211 — BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
(Common to : Computer and Communication Engineering / Computer Science and Engineering / Artificial Intelligence and Machine Learning / Artificial Intelligence and Data Science / Computer Science and Business System)

(Regulations 2023)

Time : Three Hours

Maximum : 100 Marks

Answer ALL Questions

PART A— (10x2=20 Marks)

1. State Ohm's law.
2. An Electric iron is rated 1000W, 240V. Determine the current & resistance of the heating element.
3. Write the emf equation for D.C. Generator.
4. Define voltage regulation of a transformer.
5. Why is single phase induction motor not self-starting?
6. List the applications of squirrel cage induction motor.
7. Convert the following numbers to decimals.
i) 237_8
ii) $23F_{16}$
8. List the application of Zener diode.
9. What is standard? What are the different types of standards?
10. Why instruments be calibrated?

PART B— (5x13= 65 Marks)

11. (a) Determine the currents in bridge circuit by using mesh analysis shown in Fig.11(a).

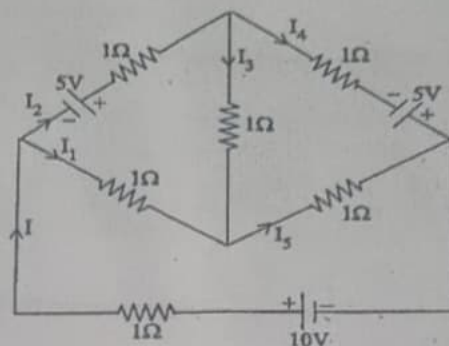


Fig.11(a)

Or

- (b) A resistor of 20Ω , inductor of $0.2H$ and a capacitor of $150\mu F$ are connected in series and fed by $230V$, $50Hz$ ac supply. Calculate (i) Inductive reactance (ii) Capacitive Reactance (iii) Impedance (iv) Current (v) Power factor (vi) Apparent power (vii) Active power (viii) Reactive power.
12. (a) With a neat sketch, explain the construction and working of DC Motor.
- Or
- (b) Brief about the construction and working of single phase transformer with a neat sketch.
13. (a) With a neat sketch, explain the Working of single phase Induction Motor.
- Or
- (b) Summarize the double revolving field theory as applied to single phase induction motor.
14. (a) i) Explain the operation of a PN Junction diode. (7)
ii) Draw the logic symbol and truth table of AND, OR and NAND gates. (6)
- Or
- (b) Examine the operation of half wave rectifier with neat sketch and derive the necessary expression.
15. (a) With neat sketch brief about the working principle of moving coil instruments.
- Or
- (b) i) Draw the block diagram of DSO and state the function of each block. (7)
ii) Write short notes on Data Acquisition. (6)

PART C — (1×15=15 Marks)

16. (a) Calculate the voltage across the 15Ω resistor in the network shown in Fig. 16(a) using nodal analysis.

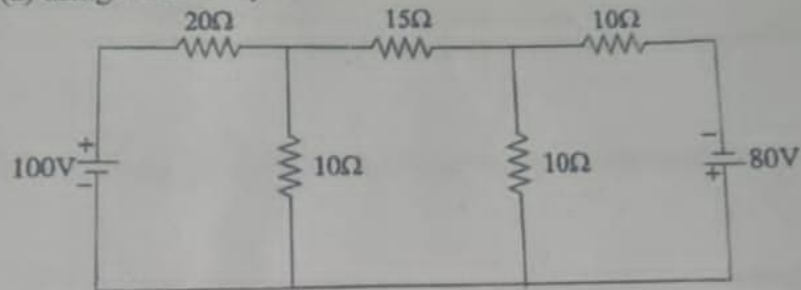


Fig. 16(a)

Or

- (b) Explain the construction and operation of Moving Iron instruments.
